

101 學年四技二專第一次聯合模擬考試

電機與電子群 專業科目（一） 詳解

101-1-03-4


101-1-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
A	A	B	A	C	C	B	D	B	B	C	C	C	A	A	A	C	B	D	B	A	C	A	A	B
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
B	D	B	C	C	B	C	D	A	A	C	C	A	A	C	B	D	B	B	A	D	B	D	D	A


第一部份：基本電學

1. $4600 \times -1.602 \times 10^{-19} = -7.36 \times 10^{-16}$ (庫倫)

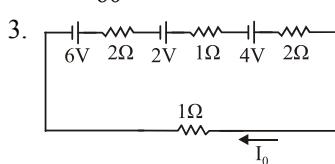2. $0.8 \times \frac{15}{60} = 0.2$ (度)(kw-hr)




故 $I_0 = \frac{12}{6} = 2$ (A)

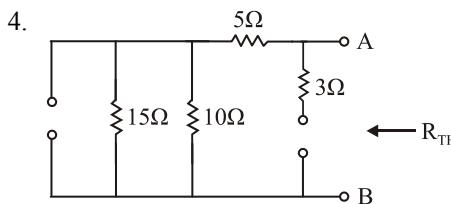

$R_{TH} = (15//10) + 5 = 11$ (Ω)

5. 達因 dyne 為力的單位， $1J = 10^7$ erg, $1\text{eV} = 1.6 \times 10^{-19}$ J

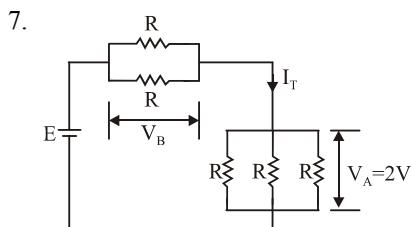6. $R = \sigma \frac{L}{A} = 1.723 \times 10^{-8} \times \frac{100}{\frac{\pi}{4} \times (1.65 \times 10^{-3})^2} = 0.806$



$I_T = \frac{2}{R} = \frac{6}{R}$, $V_B = I_T \times \frac{R}{2} = \frac{6}{R} \times \frac{R}{2} = 3$ (V)

$E = V_A + V_B = 3 + 2 = 5$ (V)


8. 設 V 點方程式

$\Rightarrow \frac{V-2}{1} + \frac{V}{1} + 1 = 0$

$V - 2 + V + 1 = 0$

$2V = 1$, $V = \frac{1}{2}$

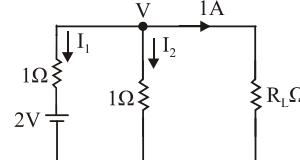故 $I_1 = -(\frac{2-\frac{1}{2}}{1}) = -1.5$ A, $I_2 = 0.5$ A




9. $I_{R1} = 6$ A, $I_{R2} = \frac{6 \times 8}{12} = 4$ A

故 $I = I_{R1} + I_{R2} + I_{R3} = 12$ A, $I_{R3} = \frac{6 \times 8}{24} = 2$ A

10. 因直流電壓源和可變電阻器與 10Ω 電阻皆為並聯，改變可變電阻的大小，並不會改變流經 10Ω 電阻的電流大小


11. $G_1 = \frac{G_b G_c + G_a G_c + G_a G_b}{G_a}$

13、14 Bus-Bar 的電路

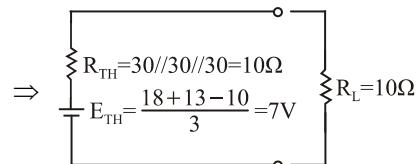當 $R_L = 10\Omega$ 時有最大功率

故 $P_{max} = \frac{E_{TH}^2}{4R_{TH}} = \frac{7^2}{4 \times 10} = \frac{49}{40} W$

15.

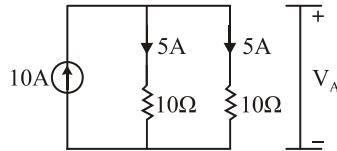三個電流源合併 $6 - 3 + 7 = 10$ A


$60\Omega // 30\Omega // 20\Omega = 10\Omega$, $V_A = 5 \times 10 = 50$ (V)

16. $\because V = I \times R$, $\therefore V \propto I$, $V \propto R$, $I \propto \frac{1}{R}$

故 $I_1 : I_2 : I_3 = \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3} = \frac{1}{1} : \frac{1}{2} : \frac{1}{3} = 6 : 3 : 2$


$V_1 : V_2 : V_3 = R_1 : R_2 : R_3 = 1 : 2 : 3$

17.

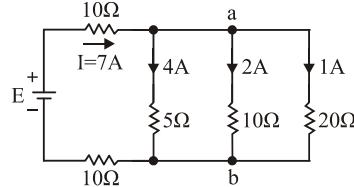

$V_{ab} = 2 \times 10 = 20$ V, $I = \frac{20}{5} + 2 + \frac{20}{20} = 7$ A

18.

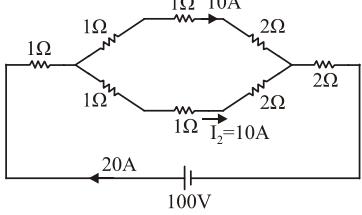


$$R_T = 1 + (1+1+2)/(1+1+2) + 2 = 5 \Omega$$

$$I = \frac{100}{5} = 20 \text{ A}, I_1 = I_2 = \frac{20}{2} = 10 \text{ A}$$

$$19. R = e \frac{\ell}{A}, R' = \frac{3}{4} R$$

$$P' = \frac{V^2}{R'} = \frac{V^2}{\frac{3}{4}R} = \frac{4}{3} \frac{V^2}{R} = \frac{4}{3} \times 600 = 800 \text{ (W)}$$

20.

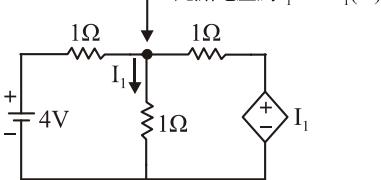


$$\text{故 } \frac{I_1 - 4}{1} + I_1 + \frac{I_1 - I_1}{1} = 0, I_1 - 4 + I_1 = 0$$

$$2I_1 = 4, I_1 = 2 \text{ (A)}$$

21. 電流 I 為最大 \Rightarrow 電阻組合要最小 \Rightarrow 故總電阻 $= R_1 // (R_2 + R_3 + R_4)$, R_1 要選擇最小的電阻

22. 由 10Ω 上方節點來看，流入等於流出，故流過 5Ω 的電流為 15 A(向左) ，故 $V_s = -10 \times 10 + 15 \times 5 = -25 \text{ V}$

23. 使用戴維寧 \Rightarrow

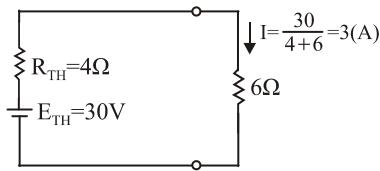

24. 此電路中 15 V 和 20 V 電壓源皆被短路(分析時)
故 $E_{TH} = (5 \times 6) + (-10) = 20 \text{ (V)}$

25. 使用重疊定理：

分析 12 V 電源時，流過 6 V 電源的電流為 4 A(向下)

分析 6 V 電源時，流過 6 V 電源的電流為 2 A(向下)

故流過 6 V 電源的總電流為 $4 \text{ A} + 2 \text{ A} = 6 \text{ A}$

6 V 電源所提供的電功率 = $6 \times 6 = 36 \text{ W}$

第二部份：電子學

26. 由圖知， $i(t) = 4 + 2 \sin \omega t$


$$\therefore I_{rms} = \sqrt{4^2 + (\frac{2}{\sqrt{2}})^2} \text{ A}$$

27. Zener 工作在逆向飽和區

28. 因 D_1 OFF, $V_o = 12 \text{ V} \times \frac{1 \text{ k}}{1 \text{ k} + 1 \text{ k}} = 6 \text{ (V)}$, $V_o < 9 \text{ V}$

故 D_2 OFF, 故 $V_o = 6 \text{ (V)}$

29.

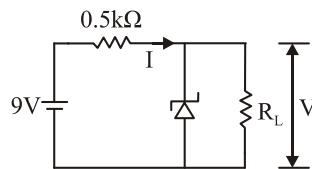

$$\begin{aligned} \text{考慮 Zener 內阻} \Rightarrow V &= V_{ZK} + r_Z \times I_{ZK} \\ &= 6.7 + 20 \times 0.2 \text{ (mA)} = 6.704 \end{aligned}$$

$$I = \frac{V - V_Z}{R} = \frac{9 - 6.704}{0.5 \text{ k}} = 4.592 \text{ (mA)}$$

$$I_{RL} = I - I_{ZK} = 4.592 - 0.2 = 4.392 \text{ (mA)}$$

$$R_{RL} = \frac{V_Z}{I_{RL}} = \frac{6.704}{4.392} = 1.52 \text{ (k}\Omega\text{)}$$

$$31. V_{dc} = \frac{2}{\pi} V_m = \frac{2}{\pi} \times 10 = \frac{20}{\pi} = 6.36 \text{ (V)}$$

$$PIV = V_m = 10 \text{ (V)}$$

$$32. V_{CC} - 0.7 = I_B R_B + (1+\beta) I_B R_B$$


$$20 - 0.7 - I_B \times 250 \text{ k} - (1+\beta) \times I_B \times 2 \text{ k} = 0$$

$$\Rightarrow 19.3 = 452 I_B \Rightarrow I_B = 0.043 \text{ (mA)}$$

$$\text{故 } I_C = \beta I_B = 4.3 \text{ (mA)}$$

33. (D) 二極體不具放大能力

34.

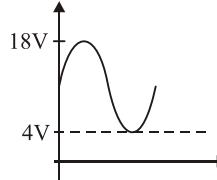

$$\text{故(A) } 4 \text{ V} \leq V_o \leq 18 \text{ V}$$

$$36. \text{ 假設全通} \Rightarrow \frac{2.4 - V}{4 \text{ k}} + \frac{3.4 - V}{2 \text{ k}} + \frac{11.4 - V}{1 \text{ k}} = \frac{V}{2 \text{ k}}$$

$$2.4 - V + 6.8 - 2V + 45.6 - 4V = 2V$$

$$\Rightarrow 9 \text{ V} = 54.8 \Rightarrow V = 6.09 \text{ (V)} \text{ (假設全通錯誤!)}$$

$$\text{故只有 } 12 \text{ V} \text{ 端導線} \Rightarrow \frac{11.4 - V_o}{1 \text{ k}} = \frac{V_o}{2 \text{ k}}$$

$$\Rightarrow 22.8 - 2V_o = V_o \Rightarrow 3V_o = 22.8 \Rightarrow \text{故 } V_o = 7.6 \text{ (V)}$$

38. 摻雜濃度大小 E > B > C, 寬度厚薄 C > E > B

$$39. \uparrow I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow \uparrow I_C = \beta I_B \uparrow \Rightarrow \downarrow V_{CE} - I_C \uparrow R_C$$

故選 A 點


$$40. I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15.7 - 0.7}{150 \text{ k}} = \frac{15}{150 \text{ k}} = 0.1 \text{ mA}$$

$$I_C = \beta I_B = 10 \text{ mA}, V_C = 15.7 - 10 \times 1 = 5.7 \text{ (V)}$$

41. 變壓器二次側為 V_m , C_3 兩端電壓為 $2V_m$

$$V_{C1} = V_m, \text{ 故 } V_{C3} = V_{C1} + V_{C2} = 2V_m$$

42.

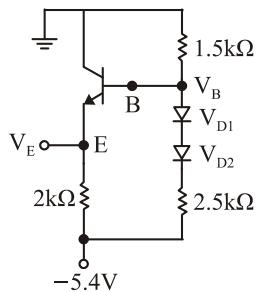

$$V_B = (-5.4 + 1.4) \times \frac{1.5 \text{ k}}{1.5 \text{ k} + 2.5 \text{ k}} = -1.5 \text{ (V)}$$

$$V_E = -1.5 - 0.7 = -2.2 \text{ (V)}$$

$$43. I_E = \frac{10 - V_{BE}}{R_E} = \frac{10 - 0.7}{20 \text{ k}} = 0.465 \text{ (mA)}$$

$$I_C = \alpha I_E = 0.46 \text{ (mA)}$$

$$44. V_{CE} = 10 - (-10) - 0.46 \times 10 \text{ k} - 0.465 \times 20 \text{ k} \\ = 20 - 4.6 - 9.3 = 6.1 \text{ (V)}$$

$$45. I_E = \frac{V_B - V_{BE}}{R_E} = \frac{5 - 0.6}{1.1 \text{ k}} = 4 \text{ mA} , I_C \cong I_E \cong 4 \text{ mA}$$

故 $V_C = -4 \text{ mA} \times 1 \text{ k}\Omega = -4 \text{ V}$

$$V_B = -10 + I_E R_E + V_{BE} \\ = -10 + 4 \text{ mA} \times 1.1 \text{ k} + 0.6 = -5 \text{ (V)}$$

因 $0 - 4 - V_{CE} - 4.4 - (-10) = 0$

\Rightarrow 故 $V_{CE} = 1.6 \text{ (V)}$

46. 硼為三價元素，加入到本質半導體中，此硼雜質稱為受體

47. (A) PN 接面的空乏區內只有正負離子
 (C) 溫度越高，其逆向飽和電流越大
 (D) 若加順向偏壓，空乏區寬度變越小

48. 代表橋式整流電路，故 V_o 頻率

$$= 2f = 2 \times 60 = 120 \text{ Hz}$$

$$49. \left. \begin{aligned} \beta_1 &= \frac{\alpha_1}{1-\alpha_1} = \frac{0.96}{0.04} = 24 \\ \beta_2 &= \frac{\alpha_2}{1-\alpha_2} = \frac{0.99}{0.01} = 99 \end{aligned} \right\}, \text{故 } \Delta\beta = 99 - 24 = 75$$

$$50. I_{C(sat)} = \frac{12 - 0.2}{1.2 \text{ k}\Omega} = 9.83 \text{ (mA)}, \text{飽和條件: } \beta I_B > I_{C(sat)}$$

$$\Rightarrow 20 \times \frac{10 - 0.7}{R_B} > 9.83 \text{ (mA)} \Rightarrow 18.92 \text{ k}\Omega > R_B$$

故答案選擇(A) 15 kΩ