

九十九學年四技二專第四次聯合模擬考試 電機與電子群 專業科目 (一) 詳解

99-4-03-4
99-4-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
D	C	C	B	A	D	A	B	A	B	C	D	D	B	A	C	B	C	A	D	D	A	B	D	C
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
C	B	A	C	B	A	D	B	D	A	C	D	A	C	C	B	D	D	C	C	A	B	B	D	B

第一部份：基本電學

1. 已知 $H = ms\Delta T = 0.24 Pt = 0.24 I^2 Rt$

其中 $m = 1000 \text{ g}$, $S = 1 \text{ 卡/g}\cdot^\circ\text{C}$, $I = 5 \text{ A}$, $R = 50 \Omega$
 $\Delta T = 32^\circ\text{C} - 20^\circ\text{C} = 12^\circ\text{C}$

$$\therefore t = \frac{ms\Delta T}{0.24 I^2 R} = \frac{1000 \text{ g} \times 1 \text{ 卡/g} \times 12^\circ\text{C}}{0.24 \times (5 \text{ A})^2 \times 50 \Omega} = 40 \text{ 秒}$$

2. 已知 $R_2 = R_1[1 + \alpha_1(T_2 - T_1)]$

其中 $R_1 = 50 \Omega$, $\alpha_1 = \alpha_{20} = \frac{0.005}{^\circ\text{C}}$

$T_2 = 60^\circ\text{C}$, $T_1 = 20^\circ\text{C}$

$$\therefore R_2 = 50 \Omega \times [1 + \frac{0.005}{^\circ\text{C}} \times (60^\circ\text{C} - 20^\circ\text{C})]$$

$$= 50 \Omega \times [1 + \frac{0.005}{^\circ\text{C}} \times 40^\circ\text{C}]$$

$$= 50 \Omega \times [1 + 0.2] = 50 \Omega \times 1.2 = 60 \Omega$$

3. 因三者為並聯，所以 2 A 電流源及 5 Ω 電阻器之兩端

電壓皆為 5 V，所以 $I_2 = \frac{5 \text{ V}}{5 \Omega} = 1 \text{ A}$

$$P_{5\Omega} = I_2^2 R = (1 \text{ A})^2 \times 5 \Omega = 5 \text{ W (消耗)}$$

$$P_{2\text{A}} = IE = 2 \text{ A} \times 5 \text{ V} = 10 \text{ W (提供)}$$


$$P_{5\text{V}} = I_1 \cdot E = (2 \text{ A} - 1 \text{ A}) \times 5 \text{ V} = 1 \text{ A} \times 5 \text{ V} = 5 \text{ W (消耗)}$$

4. 將已知電壓 ÷ 電阻得到電流如右圖，利用流入總電流 = 流出總電流即可得

$$I_{\text{流入}} = 1 \text{ A} + 4 \text{ A} + 2 \text{ A} + I = 7 \text{ A} + I$$

$$I_{\text{流出}} = 2 \text{ A} + 3 \text{ A} + 3 \text{ A} + 1 \text{ A} = 9 \text{ A}$$
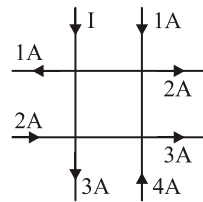
$$\therefore I = 9 \text{ A} - 7 \text{ A} = 2 \text{ A}$$




5. 藍黑金金 = $6 \Omega \pm 5\%$ (以 6 Ω 計算)，再利用 $\Delta \rightarrow Y$ 得到右圖

$$R_A = \frac{10 \times 4}{10 + 6 + 4} = 2 \Omega$$

$$R_B = \frac{10 \times 6}{10 + 6 + 4} = 3 \Omega$$

$$R_C = \frac{6 \times 4}{10 + 6 + 4} = 1.2 \Omega$$
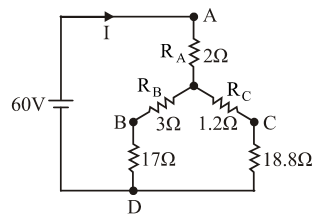
$$\therefore R_{AD} = 2 \Omega + [(3 \Omega + 17 \Omega) // (1.2 \Omega + 18.8 \Omega)] = 2 \Omega + [20 \Omega // 20 \Omega] = 2 \Omega + 10 \Omega = 12 \Omega$$



$$I = \frac{60 \text{ V}}{12 \Omega} = 5 \text{ A}$$

6. $\therefore V_B = 24 \text{ V} \times \frac{2 \Omega}{2 \Omega + 2 \Omega} = 12 \text{ V}$, $V_C = 12 \text{ V}$

$V_B = V_C$ (平衡)， $\therefore R$ 值不論為何值， I 值均保持固定 (不變)

7. 設 I_1 為單一電流，且利用電橋平衡法

$$(V_{BE} = V_{EG} = 0 \text{ V})$$

$$\text{可得 } V_{DF} = (10 + 10 + 10 + 10) \times I_1 = 40 I_1$$

$$\therefore I_2 = \frac{V_{DF}}{10 + 10} = \frac{40 I_1}{20} = 2 I_1 \text{ , 又得}$$

$$V_{AC} = 10 \Omega (I_1 + I_2) + V_{DF} + 10 \Omega (I_1 + I_2) = 30 I_1 + 40 I_1 + 30 I_1 = 100 I_1$$

$$\therefore I_3 = \frac{V_{AC}}{10 + 10} = \frac{100 I_1}{20} = 5 I_1$$

$$\text{故 } I_1 : I_2 : I_3 = I_1 : 2 I_1 : 5 I_1 = 1 : 2 : 5$$

8. (1) 當 $V_R = 0 \Omega$ 時，電路如圖(一)所示


$$I = \frac{15 \text{ V}}{10 + (10 // 10)} \times \frac{10}{10 + 10} = 0.5 \text{ A}$$

(2) 當 $V_R = \infty$ 時，電路如圖(二)所示


$$I = -I_2 = -[\frac{15 \text{ V}}{10 + (10 // (10 + 10))}] \times \frac{10}{10 + (10 + 10)} = -0.3 \text{ A}$$

故 I 值由 $-0.3 \text{ A} \sim +0.5 \text{ A}$ 變化

圖(一)

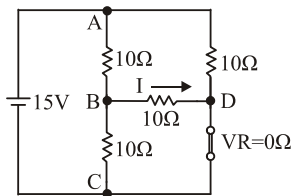

圖(二)

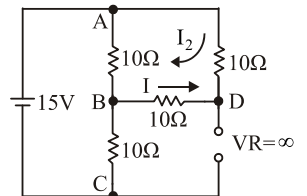

9. $P = I^2 R$, \therefore 當 $P_{\text{max}} = (0.5 \text{ A})^2 \times 10 \Omega = 2.5 \text{ W}$ 最大時 $V_R = 0 \Omega$ (注意题目的陷阱)

10. $\therefore S$ 閉合前 V_1 與 V_2 極性相反

$$\therefore \text{閉合後 } V_1 = -V_2 = \frac{Q_1 - Q_2}{C_1 + C_2} = \frac{10 \mu\text{C} - 20 \mu\text{C}}{10 \mu\text{F} + 10 \mu\text{F}}$$

$$= \frac{-10 \mu\text{C}}{20 \mu\text{F}} = -0.5 \text{ V}$$

$$11. \because e = M \frac{\Delta I}{\Delta t}, \therefore M = e \frac{\Delta t}{\Delta I} = 60 \text{ V} \times \frac{1 \text{ mS}}{2 \text{ A}} = 30 \text{ mH}$$

12. 此為兩電感並聯互消連結

$$\text{故 } L_T = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{3 \times 6 - 1^2}{3 + 6 + 2} = \frac{17}{11} \text{ H}$$

13. (1) S 閉合時, $R_{Th} = 500 \text{ k}\Omega // 500 \text{ k}\Omega = 250 \text{ k}\Omega$

$$E_{Th} = 10 \text{ V} \times \frac{500 \text{ k}\Omega}{500 \text{ k}\Omega + 500 \text{ k}\Omega} = 5 \text{ V}$$

$$\tau = R_{Th} \cdot C = 250 \text{ k}\Omega \times 1 \mu\text{F} = 250 \text{ mS} = 0.25 \text{ S}$$


$$(2) I_C = \frac{E_{Th}}{R_{Th}} \times e^{-\frac{t}{\tau}} = \frac{5 \text{ V}}{250 \text{ k}\Omega} \times e^{-\frac{1 \text{ S}}{0.25 \text{ S}}}$$

$$= 0.02 \text{ mA} \times 0.02 = 0.4 \mu\text{A}$$

$$(3) V_C = E_{Th} (1 - e^{-\frac{t}{\tau}})$$

$$= 5 \text{ V} \times (1 - e^{-\frac{1 \text{ S}}{0.25 \text{ S}}})$$
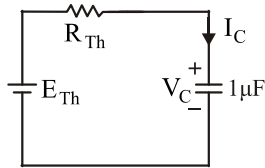
$$= 5 \text{ V} \times 0.98 = 4.9 \text{ V}$$



14. (1) $\tau_{\text{充電}} = \frac{L}{R_1} = \frac{6 \text{ H}}{2 \text{ k}\Omega} = 3 \text{ mS}$, $1 \text{ S} \gg 5 \tau_{\text{充電}}$

應為充電穩態後, $\therefore V_{L(1\text{S})} = 0 \text{ V}$

$$I_{L(1\text{S})} = \frac{E - V_{L(1\text{S})}}{R_1} = \frac{50 \text{ V} - 0 \text{ V}}{2 \text{ k}\Omega} = 25 \text{ mA}$$

\Rightarrow 視為下次放電電流的初值 $I_{L(0)}$

$$(2) \tau_{\text{放電}} = \frac{L}{R_2} = \frac{6 \text{ H}}{6 \text{ k}\Omega} = 1 \text{ mS}$$

(A) 選項錯誤 \Rightarrow 視為 $\tau = \tau_{\text{放電}} = 1 \text{ mS}$

$$(3) V_2 = V_L = -I_{L(0)} \times R_2 \times e^{-\frac{t}{\tau}}$$

$$= -25 \text{ mA} \times 6 \text{ k}\Omega \times e^{-\frac{1 \text{ mS}}{1 \text{ mS}}} = -150 \text{ V} \times 0.368 = -55.2 \text{ V}$$

$$(4) I_L = I_{L(0)} \times e^{-\frac{t}{\tau}} = 25 \text{ mA} \times e^{-\frac{1 \text{ mS}}{1 \text{ mS}}}$$

$$= 25 \text{ mA} \times 0.368 = 9.2 \text{ mA}$$

15. 已知 $f = \frac{P}{2} \times \frac{N}{60}$ (P 為極數, N 為每分鐘轉速)

$$\text{且 } P = 40, f = 60, \therefore N = \frac{120f}{P} = \frac{120 \times 60}{40} = 180 \text{ rpm}$$

$$\text{(每分鐘 180 轉), } N' = \frac{N}{60} = \frac{180}{60} = 3 \text{ rps}$$

16. (C) 互調, $CF = \sqrt{3}$, $FF = \frac{2}{\sqrt{3}}$

17. (A) $\vec{Z} = R + jX_L - jX_C$ (串聯公式)

$$= 30 - j40 \Omega = 50 \angle -53^\circ \Omega$$

$$(B) \vec{i} = \frac{v(t)}{\vec{Z}} = \frac{100\sqrt{2} \angle 30^\circ}{50 \angle -53^\circ} = 2 \angle 83^\circ \text{ A}$$

$$(C) \vec{V}_R = \vec{i} \cdot \vec{R} = 2 \angle 83^\circ \times 30 \angle 0^\circ = 60 \angle 83^\circ \Omega$$

$$(D) \vec{V}_o = \vec{i} \cdot \vec{X}_C = 2 \angle 83^\circ \times 40 \angle -90^\circ = 80 \angle -7^\circ \text{ V}$$

$$18. (A) \because \vec{V} = \vec{V}_R = \vec{V}_L = \vec{I}_L \times \vec{X}_L$$

$$= 10 \angle -90^\circ \times 10 \angle 90^\circ = 100 \angle 0^\circ$$

$$\therefore v(t) = 100\sqrt{2} \sin(\omega t + 0^\circ) = 100\sqrt{2} \sin(377t) \text{ V}$$

$$[\because \omega = 2\pi f = 2 \times 3.14 \times 60 = 377 \text{ A}]$$

$$(B) \vec{I}_R = \frac{\vec{V}_R}{R} = \frac{100 \angle 0^\circ}{10 \angle 0^\circ} = 10 \angle 0^\circ \Rightarrow$$

$$I_R = 10\sqrt{2} \sin(377t + 0^\circ) = 14.14 \sin(377t) \text{ A}$$

$$(C) \vec{I} = \vec{I}_R + \vec{I}_L = 10 \angle 0^\circ + 10 \angle -90^\circ = 10\sqrt{2} \angle -45^\circ$$

$$\Rightarrow i(t) = 20 \sin(377t - 45^\circ) \text{ A}$$

$$(D) \vec{Z} = \frac{\vec{V}}{\vec{I}} = \frac{100 \angle 0^\circ}{10\sqrt{2} \angle -45^\circ} = 5\sqrt{2} \angle 45^\circ \Omega$$

19. (A) $\because \omega = 200, \therefore X_L = \omega L = 200 \times 0.8 = 160 \Omega$

$$X_C = \frac{1}{\omega C} = \frac{1}{200 \times 25 \times 10^{-6}} = 200 \Omega, \vec{V} = 100 \angle 0^\circ$$

$$\therefore \vec{Z} = R + jX_L - jX_C = 30 + j160 - j200 = 30 - j40 \Omega$$

$$= 50 \angle -53^\circ$$

$$(B) \vec{i} = \frac{\vec{V}}{\vec{Z}} = \frac{100 \angle 0^\circ}{50 \angle -53^\circ} = 2 \angle 53^\circ \text{ A}$$

$$(C) \vec{V}_L = \vec{i} \cdot \vec{X}_L = 2 \angle 53^\circ \times 160 \angle 90^\circ = 320 \angle 143^\circ \text{ V}$$

$$(D) \vec{V}_C = \vec{i} \cdot \vec{X}_C = 2 \angle 53^\circ \times 200 \angle -90^\circ = 400 \angle -37^\circ \text{ V}$$

$$20. \because \vec{V} = \frac{100\sqrt{2}}{\sqrt{2}} \angle 30^\circ = 100 \angle 30^\circ \text{ V}$$

$$\vec{I} = \frac{10\sqrt{2}}{\sqrt{2}} \angle -30^\circ = 10 \angle -30^\circ \text{ A}$$

$$\therefore (A) \vec{S} = \vec{V} \times \vec{I}^* = 100 \angle 30^\circ \times (10 \angle -30^\circ)^*$$

$$= 100 \angle 30^\circ \times 10 \angle 30^\circ = 1000 \angle 60^\circ \text{ VA}$$

$$= 1000(\cos 60^\circ + j \sin 60^\circ) = 1000 \times \left(\frac{1}{2} + j \frac{\sqrt{3}}{2}\right)$$

$$= 500 + j500\sqrt{3} \text{ 伏安}$$

$$\text{又 } \because \vec{S} = \vec{P} + j\vec{Q} = 500 + j500\sqrt{3} \text{ VA}$$

$$= 500 \text{ W} + j500\sqrt{3} \text{ VAR}$$

$$\therefore (B) P = 500 \text{ W} = 500 \text{ 瓦特}$$

$$(C) Q = 500\sqrt{3} \text{ VAR} = 500\sqrt{3} \text{ 乏 (電感性)}$$

$$(D) P.F. = \frac{\vec{P}}{\vec{S}} = \frac{500 \angle 0^\circ}{1000 \angle 60^\circ} = 0.5 \angle -60^\circ \text{ (落後)}$$

$$21. \because \vec{Z} = R + jX_L - jX_C = 30 + j60 - j20$$

$$= 30 + j40 = 50 \angle 53^\circ \Omega$$

$$\therefore \vec{i} = \frac{\vec{V}}{\vec{Z}} = \frac{1000\sqrt{2}}{\sqrt{2}} \angle 0^\circ}{50 \angle 53^\circ \Omega} = 2 \angle -53^\circ \text{ A} = \vec{I}_R = \vec{I}_L = \vec{I}_C$$

$$(A) P = I_R^2 R = 2^2 \times 30 = 120 \text{ W}$$

$$Q = I_L^2 X_L - I_C^2 X_C = 2^2 \times 60 - 2^2 \times 20$$

$$= 240 - 80 \text{ VAR} = 160 \text{ VAR}$$

$$S = P + jQ = 120 \text{ W} + j160 \text{ VAR} = 200 \angle 53^\circ \text{ VA}$$


$$(B) P_{\text{max}} = P + S = 120 + 200 = 320 \text{ W}$$

- (C) $P_{\min} = P - S = 120 - 200 = -80 \text{ W}$
- (D) $P.F = \frac{P}{S} = \frac{120 \angle 0^\circ}{200 \angle 53^\circ} = 0.6 \angle -53^\circ$ (落後)
22. (A) 電容性 \rightarrow 電阻性 \rightarrow 電感性
23. (A) 因諧振條件 $X_L = X_C$, $\therefore B_L = B_C$
 $\therefore Y = G + jB_C - jB_L = G$ (導納最小)
- (B) $\vec{Z} = \frac{1}{\vec{Y}}$ (最大)
- (C) $\vec{I} = \frac{\vec{V}}{\vec{Z}} = \vec{V} \cdot \vec{Y}$ (最小)
- (D) \vec{V} 保持不變
24. $\vec{Z}_p = 3 + j4 \Omega = 5 \angle 53^\circ \Omega$, $V_p = \frac{V_L}{\sqrt{3}} = \frac{220\sqrt{3}}{\sqrt{3}} = 220 \text{ V}$
 $I_p = \frac{V_p}{Z_p} = \frac{220 \text{ V}}{5 \Omega} = 44 \text{ A}$
 $P_p = I_p^2 \cdot R_p = (44 \text{ A})^2 \times 3 \Omega = 5808 \text{ W}$
 $P_T = 3 P_p = 3 \times 5808 \text{ W} = 17424 \text{ W}$
25. (A) $\therefore V_p = V_L = 100 \text{ V}$, $Z_p = 100 \Omega$
 $\therefore I_p = \frac{V_p}{Z_p} = \frac{100 \text{ V}}{100 \Omega} = 1 \text{ A}$
- (B) $P = 3 I_p V_p \cos \theta = 3 \times 1 \times 100 \times \cos 60^\circ$
 $= 300 \times \frac{1}{2} = 150 \text{ W}$
- (C) $Q = 3 I_p V_p \sin \theta = 3 \times 1 \times 100 \times \sin 60^\circ$
 $= 300 \times \frac{\sqrt{3}}{2} = 150\sqrt{3} \text{ VAR}$
- (D) $S = 3 I_p V_p = 3 \times 1 \times 100 = 300 \text{ VA}$

第二部份：電子學

27. $\therefore V_o = V_Z$ 正常工作不變, $\therefore I_L = \frac{V_o}{R_L}$ 不變
 又 $\therefore I_s = \frac{V_s - V_Z}{R_s}$, 當 R_s 由小變大時, I_s 將由大變小
28. \therefore 漣波可視為三角波
 $\therefore V_{r(\text{rms})} = \frac{V_{r(\text{pp})}}{2\sqrt{3}} = \frac{6.92 \text{ V}}{2\sqrt{3}} \doteq 2 \text{ V}$
 且 $r\% = \frac{V_{r(\text{rms})}}{V_{\text{dc}}} \times 100\%$, $\therefore r\% = \frac{2 \text{ V}}{50 \text{ V}} \times 100\% = 4\%$
29. (C) 圖為倍壓電路
30. 滿足輸出波形不失真條件為 $RC \geq 5T$
 $\therefore 5T \leq RC = 2 \text{ k}\Omega \times 5 \mu\text{F} = 10 \text{ ms} \Rightarrow T \leq \frac{10 \text{ ms}}{5} = 2 \text{ ms}$
 又 $\therefore T \leq 2 \text{ ms}$, $T = \frac{1}{f} \leq 2 \text{ ms}$, $\therefore f \geq \frac{1}{2 \text{ ms}} = 500 \text{ Hz}$
31. (1) 正半週, D_1 順向導通, $V_i > 3 \text{ V}$ 時, D_2 才導通
 $V_o = V_i - 3 \text{ V}$
 (2) 負半週, D_2 順向導通, $V_i < -5 \text{ V}$ 時, D_1 才導通
 $V_o = V_i + 5 \text{ V}$
32. (A) 減少 (B) 減少 (C) 減少

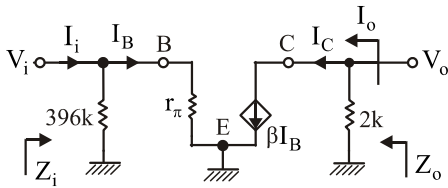33. (A) $V_C > V_B > V_E$ 工作於主動模式
 (C) $V_E > V_C > V_B$ 或 $V_C > V_E > V_B$ 工作於截止區
 (D) $V_E > V_B > V_C$ 工作於反向主動模式
34. (D) $\beta = \frac{I_C}{I_B} \times \frac{I_E}{I_E} = \frac{I_C}{I_E} \times \frac{I_E}{I_B} = \alpha \cdot \gamma$
35. (1) $I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)R_E} = \frac{12 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (1 + 100) \times 1.5 \text{ k}\Omega}$
 $= \frac{11.3 \text{ V}}{401.5 \text{ k}\Omega} \doteq 28.25 \mu\text{A}$
- (2) $I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C + R_E} = \frac{12 \text{ V} - 0.2 \text{ V}}{0.5 \text{ k}\Omega + 1.5 \text{ k}\Omega}$
 $\doteq \frac{11.8 \text{ V}}{2 \text{ k}\Omega} \doteq 5.9 \text{ mA}$
- (3) $I_{CQ} = \beta I_B = 100 \times 28.25 \mu\text{A} = 2825 \mu\text{A}$
 $= 2.83 \text{ mA} < 5.9 \text{ mA}$ 工作於線性區
- (4) $V_{CE} = V_{CC} - I_C R_C - I_E R_E \doteq V_{CC} - I_C (R_C + R_E)$
 $= 12 \text{ V} - 2.83 \text{ mA} \times (0.5 \text{ k}\Omega + 1.5 \text{ k}\Omega) = 12 \text{ V} - 5.66 \text{ V}$
 $\doteq 6.34 \text{ V}$
37. $I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C + R_E} = \frac{12 \text{ V} - 0.2 \text{ V}}{3 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{11.8 \text{ V}}{4 \text{ k}\Omega} \doteq 2.95 \text{ mA}$
- (A) $I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_C + R_E)}$
 $= \frac{12 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega + (1 + 100)(3 \text{ k}\Omega + 1 \text{ k}\Omega)} = \frac{11.3 \text{ V}}{100 \text{ k} + 404 \text{ k}}$
 $= \frac{11.3 \text{ V}}{504 \text{ k}\Omega} = 22.42 \mu\text{A}$
- (B) $I_C = \beta I_B = 100 \times 22.42 \mu\text{A} = 2.242 \text{ mA}$
- (C) $V_C = V_{CC} - (1 + \beta)I_B R_C$
 $= 12 \text{ V} - (1 + 100) \times 22.42 \mu\text{A} \times 3 \text{ k}\Omega$
 $= 12 \text{ V} - 6.79 \text{ V} = 5.21 \text{ V}$
- (D) $V_E = (1 + \beta)I_B R_E = (1 + 100) \times 22.42 \mu\text{A} \times 1 \text{ k}\Omega$
 $= 2.264 \text{ V} \doteq 2.3 \text{ V}$
38. $V_o = V_E - V_{BE} = 5 \text{ V} - 0.7 \text{ V} \approx 4.3 \text{ V}$
39. $\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{11 \text{ V} - 0.7 \text{ V}}{396 \text{ k}\Omega} = \frac{10.3 \text{ V}}{396 \text{ k}\Omega}$
 $\doteq 26 \mu\text{A}$, $\therefore r_\pi = \frac{V_T}{I_B} = \frac{26 \text{ mV}}{26 \mu\text{A}} \doteq 1 \text{ k}\Omega$
- (A) $A_i = \frac{I_o}{I_i} = \frac{\beta I_B}{\frac{396 \text{ k} + 1 \text{ k}}{396 \text{ k}} I_B} \doteq \beta \doteq 100$
- (B) $A_V = \frac{V_o}{V_i} = \frac{-\beta I_B R_C}{I_B r_\pi} = \frac{-100 \times I_B \times 2 \text{ k}\Omega}{I_B \times 1 \text{ k}\Omega} \doteq -200$
- (C) $Z_o = 2 \text{ k}\Omega$
- (D) $Z_i = 396 \text{ k} // 1 \text{ k}\Omega \doteq 1 \text{ k}\Omega$



40. $\therefore \frac{V_o}{V_i} = \frac{I_o}{I_i} \times \frac{Z_o}{Z_i}$, $\therefore Z_i = \frac{I_o}{I_i} \times \frac{V_i}{V_o} \times Z_o = A_i \times \frac{1}{A_v} \times Z_o$
 $= 50 \times \frac{1}{500} \times 5 \text{ k}\Omega = \frac{1}{2} \text{ k}\Omega$

41. (A) $\beta_1 \beta_2 R_E \div \beta^2 R_E$
 (C) 低, 1
 (D) 高, β^2

42. 當 $V_{GS} = 0 \text{ V}$ 時, $I_D = I_{DSS}(1 - \frac{V_{GS}}{V_p})^2$
 $= 18 \text{ mA} \times (1 - \frac{0 \text{ V}}{-3 \text{ V}})^2 = 18 \text{ mA} \times (1 - 0)^2 = 18 \text{ mA}$
 $\therefore V_{GS} = -4 \text{ V}$ 已超出 $V_p = -3 \text{ V}$ 被截止
 $\therefore I_D = 0 \text{ mA}$


43. $I_D = k(V_{GS} - V_T)^2 = 0.3 \text{ mA/V}^2 \times (5 \text{ V} - 2 \text{ V})^2$
 $= 0.3 \times 3^2 = 2.7 \text{ mA}$

44. (1) $V_{GS} = V_G - V_S = I_G R_G - I_S R_S$ ($\because I_S = I_D$)
 $= 0 \times R_G - I_D R_S = 0 - 1.5 \text{ mA} \times 1 \text{ k}\Omega = -1.5 \text{ V}$
 $g_m = \frac{2 I_{DSS}}{|V_p|} \times (1 - \frac{V_{GS}}{V_p}) = \frac{2 \times 12 \text{ mA}}{|-3 \text{ V}|} \times (1 - \frac{-1.5 \text{ V}}{-3 \text{ V}})$
 $= \frac{2 \times 12}{3} \times (1 - \frac{1}{2}) = 4 \text{ mS}$

(2) $Z_i = R_G = 1 \text{ M}\Omega$, $Z_o = R_D = 4 \text{ k}\Omega$

(3) $A_v = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-4 \text{ mS} \times 4 \text{ k}\Omega}{1 + 4 \text{ mS} \times 1 \text{ k}\Omega} = \frac{-16}{1 + 4} = \frac{-16}{5}$
 $= -3.2$

(4) $A_i = |A_v| \times \frac{Z_i}{R_D} = 3.2 \times \frac{1 \text{ M}\Omega}{4 \text{ k}\Omega} \div 800$

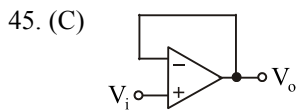

46. 此為非反相放大器 $V_o = (1 + \frac{R_1}{R_2}) V_i$

$\therefore V_o = (1 + \frac{6 \text{ k}\Omega}{6 \text{ k}\Omega}) \times 6 \sin 377t = 12 \sin 377t$

47. ① 先求上下臨界電壓

$V_+ = \frac{2 \text{ k}}{2 \text{ k} + 4 \text{ k}} (+12 \text{ V}) = 4 \text{ V}$

$V_- = \frac{2 \text{ k}}{2 \text{ k} + 4 \text{ k}} (-12 \text{ V}) = -4 \text{ V}$

② 可求電容兩端峰對峰電壓

$\therefore V_{C(P-P)} = 4 \text{ V} - (-4 \text{ V}) = 8 \text{ V}$

48. $\therefore \beta A = 1 \angle 0^\circ = 1 \angle 360^\circ$ 且 $A = 10 \angle 150^\circ$

$\therefore \beta = \frac{1 \angle 0^\circ}{10 \angle 150^\circ} = 0.1 \angle -150^\circ$ 或 $0.1 \angle 210^\circ$

49. 此為反相舒密特電路, 且上下限臨界電壓為

$V_u = +12 \text{ V} \times \frac{R_1}{R_1 + R_2} = +6 \text{ V}$

$V_L = -12 \text{ V} \times \frac{R_1}{R_1 + R_2} = -6 \text{ V}$

為正弦波之波峰與波谷, 可以使 OPA 符合轉態故輸出為相同頻率之方波

50. $T = 0.693(R_{B1}C_1 + R_{B2}C_2) = 0.693(R_2C_1 + R_3C_2)$