

九十八學年四技二專第四次聯合模擬考試 電機與電子群 專業科目 (一) 詳解

98-4-03-4
98-4-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
B	D	A	A	C	D	D	D	B	B	C	C	B	A	D	A	C	B	C	B	B	C	A	A	D
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
A	C	D	C	C	C	D	D	A	C	B	A	C	A	C	A	D	B	D	C	D	B	D	B	D

第一部份：基本電學

1. (B) $\bar{Z} = 2 + 3 + \frac{45^2(1+j)(1-j)}{45(1+j+1-j)} = 50 \Omega$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{100 \angle 60^\circ}{50 \angle 0^\circ} = 2 \angle 60^\circ \text{ A}$$


2. $|\bar{I}_1| = \frac{100}{10} = 10 \text{ A}$, $|\bar{I}_2| = \frac{100}{20} = 5 \text{ A}$

$$|\bar{I}_3| = \frac{100}{\sqrt{6^2 + 8^2}} = 10 \text{ A}$$

$$P_T = I_1^2 \times 10 + I_3^2 \times 6 = 10^2 \times 10 + 10^2 \times 6 = 1600 \text{ W}$$

$Q_T = I_2^2 \times 20 - I_3^2 \times 8 = 5^2 \times 20 - 10^2 \times 8 = 300 \text{ VAR}$ (電容性), 當 $Q_L = Q_C$ 時, 電路呈純電阻性
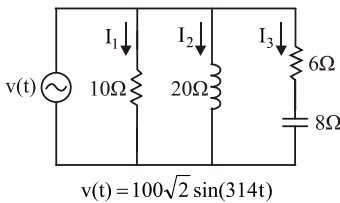
$$\frac{100^2}{X_L} = 800 \Rightarrow X_L = \frac{10000}{800} = 12.5 \Omega$$



3. (1) $|\bar{I}| = \left| \frac{\bar{V}_{R1}}{12} \right| = \frac{24}{12} = 2 \text{ A}$

$$\Rightarrow |\bar{Z}| = \left| \frac{\bar{V}}{\bar{I}} \right| = \frac{96\sqrt{2}}{2} = 48\sqrt{2} \Omega$$


(2) 由於總功因為 0.707 落後, 即 $\theta_Z = \theta_V - \theta_I = 45^\circ$

(3) 由上兩式得知總阻抗

$$\bar{Z} = 48\sqrt{2} \angle 45^\circ = 48 + j48 = A + jB$$

$$\text{故得 } A = B = 48 \frac{A}{4} + B = \frac{48}{4} + 48 = 60$$

4.

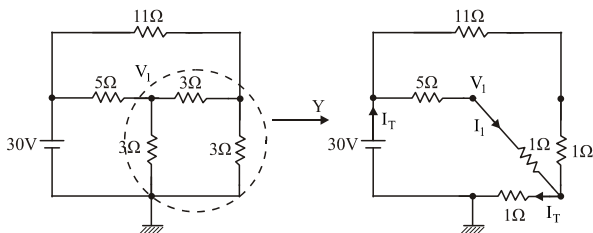


$$I_T = \frac{30}{1 + (6//12)} = 6 \text{ A} \Rightarrow V_1 = I_1 \times 1 + I_T \times 1$$

$$= (6 \times \frac{12}{12+6} \times 1) + (6 \times 1) = 10 \text{ V}$$

5. $\bar{Z} = 30 // j40 // -j20 = 19.2 - j14.4 = 24 \angle -37^\circ \Omega$

故電路為電容性 $\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 30^\circ}{24 \angle -37^\circ} = 5 \angle 67^\circ \text{ A}$


6. (1)

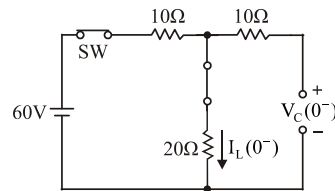

穩態時, 可求得 $I_L(0^-) = \frac{60}{30} = 2 \text{ A}$

且 $V_C(0^-) = 2 \times 20 = 40 \text{ V}$

(2)

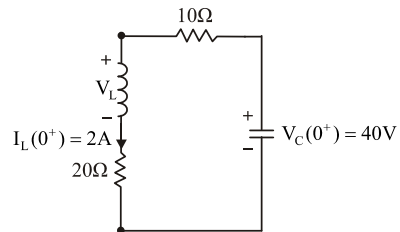


開關打開瞬間, 可得 $V_L = -2 \times (20 + 10) + 40 = -20 \text{ V}$

7. $e = L \frac{\Delta i}{\Delta t} = 10 \times \frac{14 - 4}{8 - 3} = 20 \text{ V}$

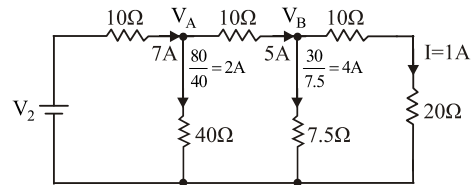8. 利用單位電流法: $V_A = 5 \times 10 + 30 = 80 \text{ V}$

$$V_B = 1 \times (10 + 20) = 30 \text{ V}, V_2 = 7 \times 10 + 80 = 150 \text{ V}$$




$$9. V_{av} = \frac{1}{3\pi} (6 \times 3\pi - \frac{1}{2} \times 6 \times \pi - \frac{2}{\pi} \times 3 \times \pi)$$


$$= \frac{18\pi - 3\pi - 6}{3\pi} = 5 - \frac{2}{\pi} = 4.36 \text{ A}$$

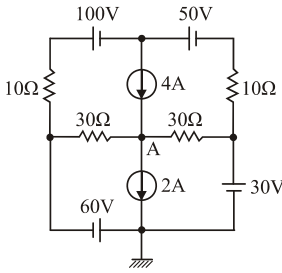11. 利用密爾門定理

$$V_A = (-\frac{60}{30} - 2 + 4 + \frac{30}{30}) \times (30 // 30) = 15 \text{ V}$$




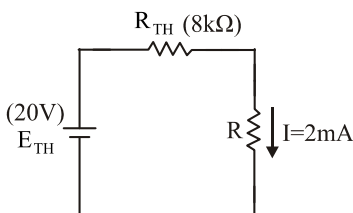12. $W = Q \times (V_A - 20) \Rightarrow -40 = -5 \times (V_A - 20)$
 $\Rightarrow V_A = 28 \text{ V}$ ，故知為逆電場移動
13. (B) 本題為並聯運轉，故必須算出總輸入功率
 故得 $h = \frac{P_O}{P_I} = \frac{746 + 1000}{\frac{746}{0.746} + \frac{1000}{0.8}} = \frac{1746}{2250} = 0.78$
14. $\bar{I} = \frac{600 \angle 90^\circ - 600 \angle 30^\circ}{80 - j60} = \frac{j600 - 300\sqrt{3} - j300}{80 - j60}$
 $= \frac{-300\sqrt{3} + j300}{80 - j60} = 6 \angle 187^\circ \text{ A}$
15. (D) \cos 函數在零度時最大
 所以 $\frac{1000}{3} \pi t - \frac{\pi}{3} = 0^\circ \Rightarrow t = 1.0 \text{ ms}$
16. $V_\ell = 100\sqrt{3} \text{ A}$ ， $I_\ell = \frac{\left(\frac{100\sqrt{3}}{\sqrt{3}}\right)}{\sqrt{8^2 + 6^2}} = 10 \text{ A}$
 $\cos \theta_z = \frac{4}{5}$ ， $\theta_z = 37^\circ$ ， $P = \sqrt{3} V_\ell I_\ell \cos \theta_z$
 $= \sqrt{3} \times (100\sqrt{3}) \times (10) \times \cos 37^\circ = 2400 \text{ W}$
17. I_3 迴路： $6I_1 + 4I_2 + 12I_3 = 32$
18. 利用密爾門定理得 $V_Y = \left(\frac{8}{3} + \frac{6}{1} - 6\right) \times (3 // 1) = 2 \text{ V}$
19. (A) $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{4 \times 10^{-3} \times 1 \times 10^{-3}}} = 80 \text{ Hz}$
 (B) $Q_P = R\sqrt{\frac{C}{L}} = 40\sqrt{\frac{1 \text{ m}}{4 \text{ m}}} = 20 \Rightarrow$
 $B.W. = \frac{f_r}{Q_P} = \frac{80}{20} = 4 \text{ Hz}$
 (C) $\because Q_P > 15 \Rightarrow \therefore f_H = f_r + \frac{B.W.}{2} = 80 + \frac{4}{2} = 82 \text{ Hz}$
 此為半功率點，故 $P = \frac{P_r}{2} = \frac{10^2 \times 40}{2} = 2 \text{ kW}$
 (D) 當電阻增加時，品質因數會增加，故頻寬會減少
20. $W_C = \frac{1}{2} \times 10 \times 10^{-6} (50^2 - 40^2) = 4500 \text{ mJ}$
- 21.



將電路化簡成戴維寧等效

- $E_{TH} = 60 \times \frac{12}{12+6} - 60 \times \frac{6}{12+6} = 20 \text{ V}$
 $R_{TH} = (6 \text{ k} // 12 \text{ k}) + (6 \text{ k} // 12 \text{ k}) = 8 \text{ k}\Omega$
 $R_T = \frac{20}{2 \text{ m}} = 10 \text{ k}\Omega = R_{TH} + R \Rightarrow R = 2 \text{ k}\Omega$
22. 由於最大功率轉移時
 $R_L = R_{TH} \Rightarrow 4 = 5 // (10 + R) \Rightarrow R = 10 \Omega$
23. (1) $\alpha_{40} = 0.004 = \frac{1}{250} = \frac{1}{T+40} \Rightarrow T = 210^\circ \text{C}$
 (2) $\alpha_{-10} = \frac{1}{T-10} = 0.005$
24. (1) $1T = 10^4 \text{ Gauss} \Rightarrow 10^5 \text{ Gauss} = 10 \text{ T}$
 (2) $\mu = \frac{B}{H} = \frac{10}{800} = 12.5 \times 10^{-3} \left(\frac{\text{H}}{\text{m}}\right)$
25. $V_A = \left(\frac{0}{12} + 5 + \frac{24}{6}\right) \times (12 // 6)$
 $= 9 \times 4 = 36 \text{ V}$
 $I_1 = \frac{36}{12} = 3 \text{ A}$
 $I_5 = 5 - I_1 = 5 - 3 = 2 \text{ A}$
 $I_4 = \frac{24 + 10}{17} = 2 \text{ A}$
 $I_2 = I_5 - I_4 = 2 - 2 = 0 \text{ A}$
 $I_3 = 5 - I_4 = 5 - 2 = 3 \text{ A}$
 $I_1 + I_2 + I_3 = 3 + 0 + 3 = 6 \text{ A}$

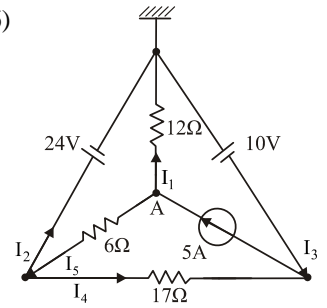

第二部份：電子學

28. 二極體加逆偏後，空乏區內電場方向由 N 指向 P 側，且漏電流大小不隨逆向偏壓大小改變
29. $D_1 \rightarrow \text{ON}$ ， $D_2 \rightarrow \text{OFF}$ ，故 $V_o = -2.5 \text{ V}$
30. 當輸入 $V_i = 30 \text{ V} \sim 70 \text{ V}$ 時輸出隨輸入變化
 故 $V_o = \frac{\frac{V_i}{100 \text{ k}} + \frac{30}{200 \text{ k}}}{\frac{1}{100 \text{ k}} + \frac{1}{200 \text{ k}}} = \frac{2}{3} V_i + 10$ ， $A = \frac{2}{3}$ 、 $B = 10$
31. $I_{Z(\text{max})} = \frac{P_D}{V_Z} = \frac{50 \text{ mW}}{5} = 10 \text{ mA}$
 $V_{I(\text{min})} = 200 \times \left(1 \text{ m} + \frac{5}{250}\right) + 5 = 9.2 \text{ V}$
 $V_{I(\text{max})} = 200 \times \left(10 \text{ m} + \frac{5}{250}\right) + 5 = 11 \text{ V}$
32. FET 為單載子元件，故溫度升高時，主要載子的碰撞機率增加，汲極電流下降，故不會產生熱跑脫
33. Q_1 、 Q_3 、 Q_4 、 Q_5 共四個
34. $I_C = \alpha I_E = \frac{\beta}{1+\beta} \times I_E = \frac{50}{1+50} \times 1 \text{ mA} = 0.98 \text{ mA}$
35. $I_C = \beta I_B + (1+\beta) I_{CBO} \Rightarrow 10 \text{ mA}$
 $= \beta \times \frac{5.7 - 0.7}{500 \text{ k}} + 0.1 \text{ mA} \Rightarrow \beta = 990$

36. 當 $V_{CEQ} = \frac{1}{2} V_{CC}$ 時, 可得最大不失真輸出

故 $I_{CQ} = \frac{5}{1k} = 5 \text{ mA}$


37. $I_D = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2 \Rightarrow 4 \text{ mA} = 9 \text{ mA} \times (1 - \frac{V_{GS}}{-3})^2$

$\Rightarrow V_{GS} = -1 \text{ V}$

$V_{GS} = V_G - V_S \Rightarrow -1 = 5 - V_S \Rightarrow V_S = 6 \text{ V}$

故 $V_{DS} = 11 - 6 = 5 \text{ V}$

38. $Z_o = Z_o' // r_o = r_e // r_o$

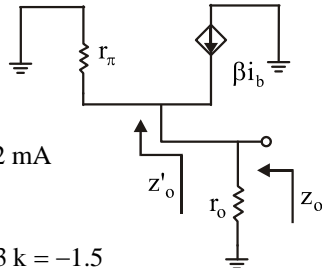

39. $I_D = I_S = I_E = \frac{10 - 0.6}{4.7k} = 2 \text{ mA}$

$V_D = 15 - 2 \text{ mA} \times 3k = 9 \text{ V}$

40. $A_V = -g_m R_D = -500 \mu \times 3k = -1.5$

41. $I_{B1} = \frac{I_{C2}}{\beta^2} = \frac{100 \text{ mA}}{100^2} = 0.01 \text{ mA}$, $r_{\pi1} = \frac{25 \text{ m}}{0.01 \text{ m}} = 2.5 \text{ k}\Omega$

$r_{\pi2} = \frac{25 \text{ m} \times 100}{100 \text{ m}} = 25 \Omega$

$P_C = I_C \times V_{CE}$ 又 $I_{C2} \gg I_{C1}$, 故 $P_{C1} < P_{C2}$

$r_{\pi2} \cong \frac{V_T}{I_{C2}} \times \beta = \frac{25 \text{ m}}{100 \text{ m}} \times 100 = 25 \Omega$

$r_{\pi1} \cong \frac{V_T}{I_{E1}} \times \beta = \frac{25 \text{ m}}{1 \text{ m}} \times 100 = 2.5 \text{ k}\Omega$


42. $f = \frac{1}{0.7 \times (10k + 10k) \times 1 \mu} = \frac{1}{14 \text{ m}} \times 71.4 \text{ Hz}$

工作週期(DC%) = $\frac{10k}{10k + 10k} \times 100\% = 50\%$

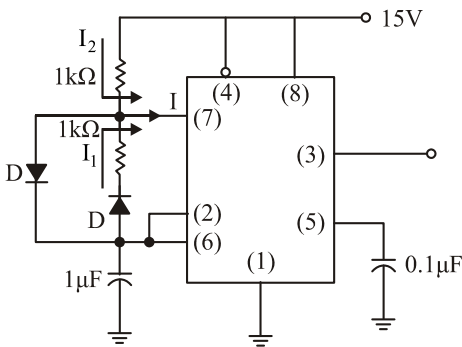43. $I = \frac{\frac{2}{3} \times 15 - 0.6 - 0.2}{10k} = 0.92 \text{ mA}$

$I_2 = \frac{15 - 0.2}{10k} = 1.48 \text{ mA}$

$I = I_1 + I_2 = 0.92 \text{ m} + 1.48 \text{ m} = 2.4 \text{ mA}$



44. $V_{o1} = -V_1 \times \frac{20k}{10k} = -2 \times 2 = -4 \text{ V}$

$V_o = -V_{o1} \times \frac{20k}{20k} = -(-4) \times 1 = 4 \text{ V}$

45. $5 \geq 400 \text{ m} \times \frac{R_x}{15k + R_x} \times (1 + \frac{63k}{4.5k})$

$15k + R_x = 1.2R_x \Rightarrow 0.2R_x = 15k \Rightarrow R_x = 75k\Omega$

46. $\frac{0 - 10}{10k} + \frac{0 - V_{TL}}{10} + \frac{0 - 10}{1k} = 0$


$-1 \text{ m} - \frac{V_{TL}}{10} - 10 \text{ m} = 0 \Rightarrow V_{TL} = -110 \text{ mV}$

$\frac{0 - 10}{10k} + \frac{0 - V_{TH}}{10} + \frac{0 - (-10)}{1k} = 0$

$-1 \text{ m} - \frac{V_{TH}}{10} + 10 \text{ m} = 0 \Rightarrow V_{TH} = 90 \text{ mV}$

$V_H = V_{TH} - V_{TL} = 90 \text{ m} - (-110 \text{ m}) = 200 \text{ mV}$

47.

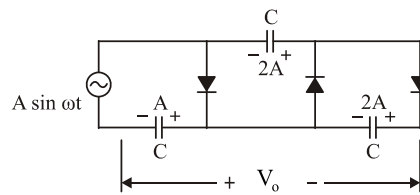

故 $V_o = -3 \text{ A}$

48. $V_o = -3 \times \frac{10k}{5k} = -6 \text{ V}$

49. $\beta \times A_V = 1 \angle 0^\circ$

$\Rightarrow \beta \times 10 \angle 173^\circ = 1 \angle 0^\circ$

故 $\beta = 0.1 \angle 187^\circ$

50. $\beta A_V > 1$ 會產生減幅振盪
 V_o 最終會無輸出

